

Assignment Submission Sheet

Term: 321221

Submission Date: 22-11-2021

Assignment Number: 05

Course Code: ECE290

Section: E1901

Group: A

Registration Number: 11904463

Student Name: Mohit Rawat

Roll No: 09

1. Concept Learned

I have learn about how to make 16 x 1 Multiplexer using 4 x 1 multiplexer and how to code in Verilog and make simulation of it.

2. Key Observations & Insights

Key observation is the output waveform was the multiplexer's output according to select line and the input given throw testbench.

3. Application Areas

Application of Multiplexer is in modern devices like microprocessor inside ALU.

4. A Verilog Program to implement 16 x 1 Multiplexer using 4 x 1 Multiplexers.



4x1 Multiplexer.

Truth table:-

I_3	I_2	I_1	I_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

S_1	S_0	Out
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Circuit Diagram of 4×1 Mux.

  


16 X 1 Multiplexer using 4 X 1 Multiplexer

Truth Table

S_3	S_2	S_1	S_0	Out
0	0	0	0	I_0
0	0	0	1	I_1
0	0	1	0	I_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	I_7
1	0	0	0	I_8
1	0	0	1	I_9
1	0	1	0	I_{10}
1	0	1	1	I_{11}
1	1	0	0	I_{12}
1	1	0	1	I_{13}
1	1	1	0	I_{14}
1	1	1	1	I_{15}

Circuit Diagram. 18x1

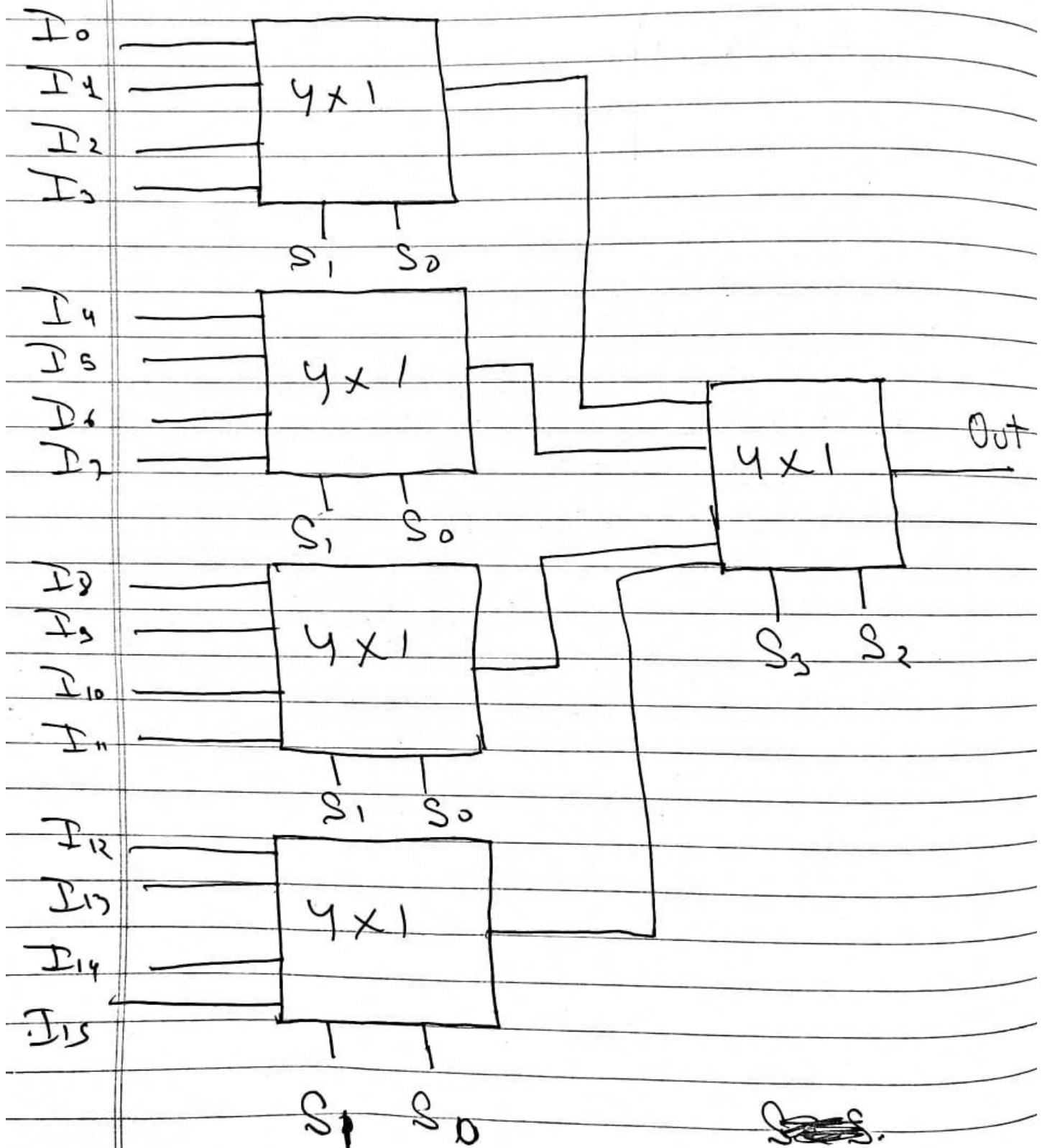



Verilog Code



```
1  `timescale 1ns / 1ps
2
3  module Mux_4x1(I, S, O);
4  input I;
5  wire [3:0] I;
6  input S;
7  wire [1:0] S;
8
9  output O;
10 reg O;
11
12
13 always @ (I or S)
14 begin
15     if(S == 2'b00)
16         O <= I[0];
17     else if(S == 2'b01)
18         O <= I[1];
19     else if(S == 2'b10)
20         O <= I[2];
21     else if(S == 2'b11)
22         O <= I[3];
23 end
24
25 endmodule
26
27
28 module Mux_16x1(I, S, O);
29 input [15:0] I;
30 input [3:0] S;
31 output O;
32
33 wire [3:0] w;
34
35 Mux_4x1 M4_1(I[3:0], S[1:0], w[0]);
36 Mux_4x1 M4_2(I[7:4], S[1:0], w[1]);
37 Mux_4x1 M4_3(I[11:8], S[1:0], w[2]);
38 Mux_4x1 M4_4(I[15:12], S[1:0], w[3]);
39
40 Mux_4x1 M4_5(w, S[3:2], O);
41
42 endmodule
43
```


Test Bench For Verilog Code

```
1  `timescale 1ns / 1ps
2
3
4  module Mux_16x1_TB_v;
5
6      // Inputs
7      reg [15:0] I;
8      reg [3:0] S;
9
10     // Outputs
11     wire O;
12
13     // Instantiate the Unit Under Test (UUT)
14     Mux_16x1 uut (
15         .I(I),
16         .S(S),
17         .O(O)
18     );
19
20     initial begin
21         // Initialize Inputs
22         I = 0;
23         S = 0;
24         // Wait 100 ns for global reset to finish
25         #5;
26
27         I=16'b0000000000000001; S=4'b0000; #10;
28         I=16'b0000000000000010; S=4'b0001; #10;
29         I=16'b0000000000000100; S=4'b0010; #10;
30         I=16'b0000000000001000; S=4'b0011; #10;
31         I=16'b0000000000100000; S=4'b0100; #10;
32         I=16'b0000000001000000; S=4'b0101; #10;
33         I=16'b0000000010000000; S=4'b0110; #10;
34         I=16'b0000000100000000; S=4'b0111; #10;
35         I=16'b0000001000000000; S=4'b1000; #10;
36         I=16'b0000010000000000; S=4'b1001; #10;
37         I=16'b0000100000000000; S=4'b1010; #10;
38         I=16'b0001000000000000; S=4'b1011; #10;
39         I=16'b0010000000000000; S=4'b1100; #10;
40         I=16'b0100000000000000; S=4'b1101; #10;
41         I=16'b1000000000000000; S=4'b1110; #10;
42         I=16'b1000000000000000; S=4'b1111; #10;
43     end
44 endmodule
45
46
```


Schematic Diagram

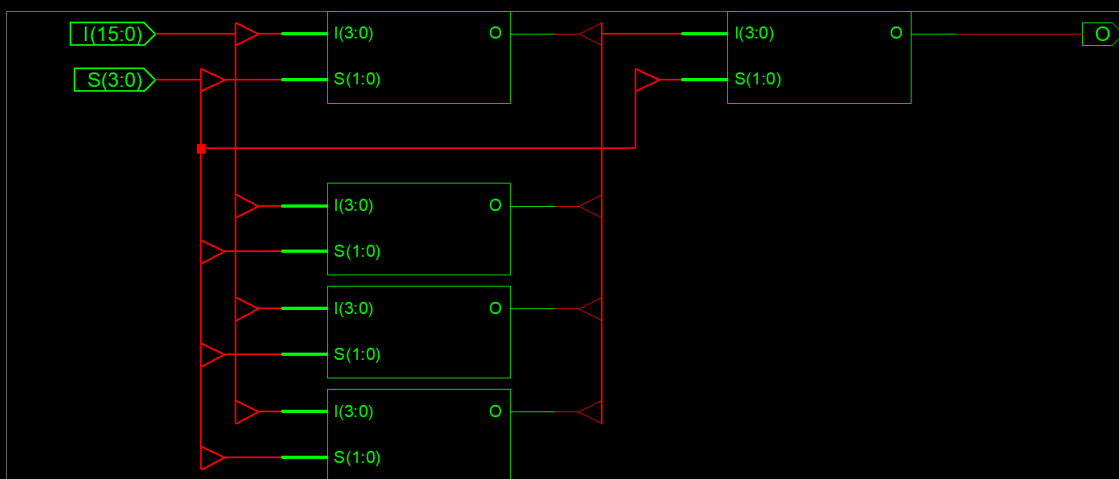 

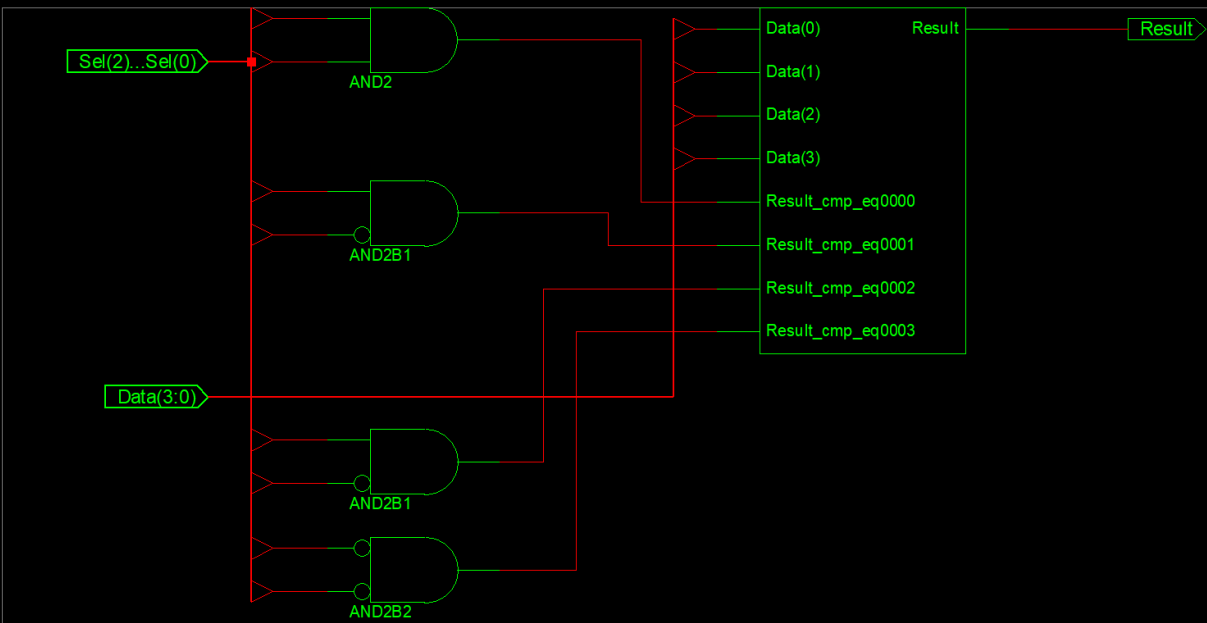 

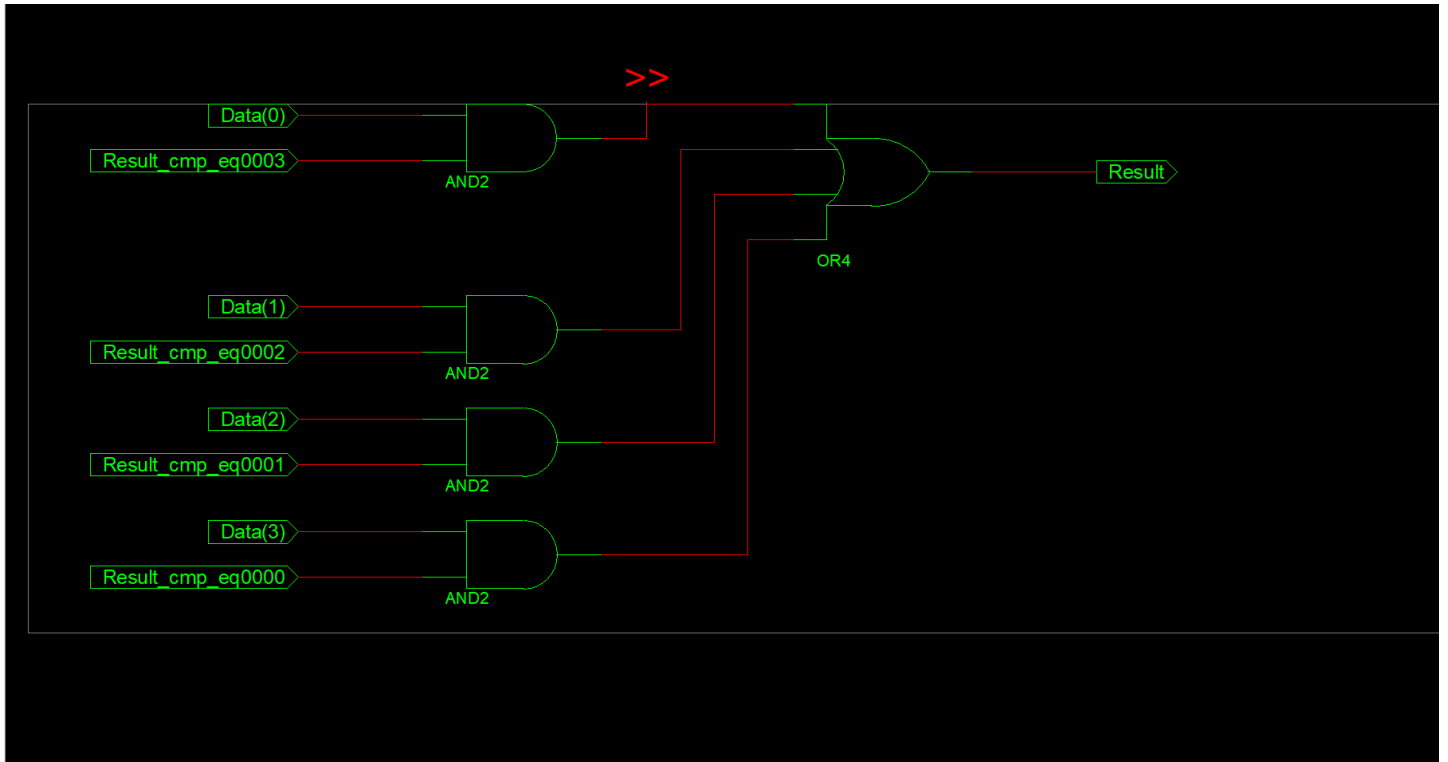

Wave Form

 

END