

Assignment Submission Sheet

Term: 321221

Submission Date: 02-11-2021

Assignment Number: 04

Course Code: ECE290

Section: E1901

Group: A

Registration Number: 11904463

Student Name: Mohit Rawat

Roll No: 09

1. Concept Learned

I have learn about how to make 4 bit up counter using verilog and how to make testbench and give clock in circuit.

2. Key Observations & Insights

Key observation is the output waveform was that it start from 0000 and count up to 1111 and again starting from 0000.


3. Application Areas

Application of counter is in many digital machine like washing machine, micro owner, program counter in computer.

4. A verilog Program to implement 4 bit synchronous Up counter using D- Flip Flop.

Q \Rightarrow A verilog program to implement 4-bit Synchronous up counter using D FF.

Sol \Rightarrow State diagram:-

 

Excitation table of D Flip Flop:-

Q	Q _{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation table of 4-bit Up counter using DFF.

	Present State				Next State				FF input			
	Q_3	Q_2	Q_1	Q_0	$Q_3(t+1)$	$Q_2(t+1)$	$Q_1(t+1)$	$Q_0(t+1)$	D_3	D_2	D_1	D_0
0	0	0	0	0	0	0	0	1	0	0	0	1
1	0	0	0	1	0	0	1	0	0	0	1	0
2	0	0	1	0	0	0	1	1	0	0	1	1
3	0	0	1	1	0	1	0	0	0	1	0	0
4	0	1	0	0	0	1	0	1	0	1	0	1
5	0	1	0	1	0	1	1	0	0	1	1	0
6	0	1	1	0	0	1	1	1	0	1	1	1
7	0	1	1	1	1	0	0	0	1	1	0	0
8	1	0	0	0	1	0	0	1	1	0	0	1
9	1	0	0	1	1	0	1	0	1	0	1	0
10	1	0	1	0	1	0	1	1	1	0	1	1
11	1	0	1	1	1	1	0	0	1	1	0	0
12	1	1	0	0	1	1	0	1	1	1	0	1
13	1	1	0	1	1	1	1	0	1	1	1	0
14	1	1	1	0	1	1	1	1	1	1	1	1
15	1	1	1	1	0	0	0	0	0	0	0	0

K-map For FF Inputs.

K-map D_3 :-

$d_3 d_2$ \ $d_1 d_0$		00	01	11	10
		00	01	11	10
00	0	0	0	0	0
01	0	0	0	1	0
11	1	1	0	0	1
10	1	1	1	1	1

$$\begin{aligned}
 D_3 &= \bar{d}_3 \bar{d}_2 + \bar{d}_3 \bar{d}_1 + \bar{d}_3 \bar{d}_0 + \bar{d}_3 d_2 d_1 d_0 \\
 &= \bar{d}_3 (\bar{d}_2 + \bar{d}_1 + \bar{d}_0) + \bar{d}_3 (d_2 d_1 d_0) \\
 &= \bar{d}_3 (d_2 d_1 d_0)' + \bar{d}_3 (d_2 d_1 d_0)
 \end{aligned}$$

$$D_3 = \bar{d}_3 \oplus (d_2 d_1 d_0)$$

Kmap - D_2

$d_3 d_2 \backslash d_1 d_0$

	00	01	11	10
00	0	0	1	0
01	1	1	0	1
11	1	1	0	1
10	0	0	1	0

$$\begin{aligned}
 D_2 &= d_2 \bar{d}_1 + d_2 \bar{d}_0 + \bar{d}_2 d_1 d_0 \\
 &= d_2 (\bar{d}_1 + \bar{d}_0) + \bar{d}_2 (d_1 d_0) \\
 &= d_2 (\overline{d_1 d_0}) + \bar{d}_2 (d_1 d_0)
 \end{aligned}$$

$$D_2 = d_2 \oplus (d_1 d_0)$$

Kmap - D_1

$Q_3 Q_2$	$Q_1 Q_0$			
	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$D_1 = \bar{Q}_1 Q_0 + Q_1 \bar{Q}_0$$


$$D_1 = Q_1 \oplus Q_0$$

Kmap - D_0

$Q_3 Q_2$	$Q_1 Q_0$			
	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

$$D_0 = \bar{Q}_0$$

Circuit Design.

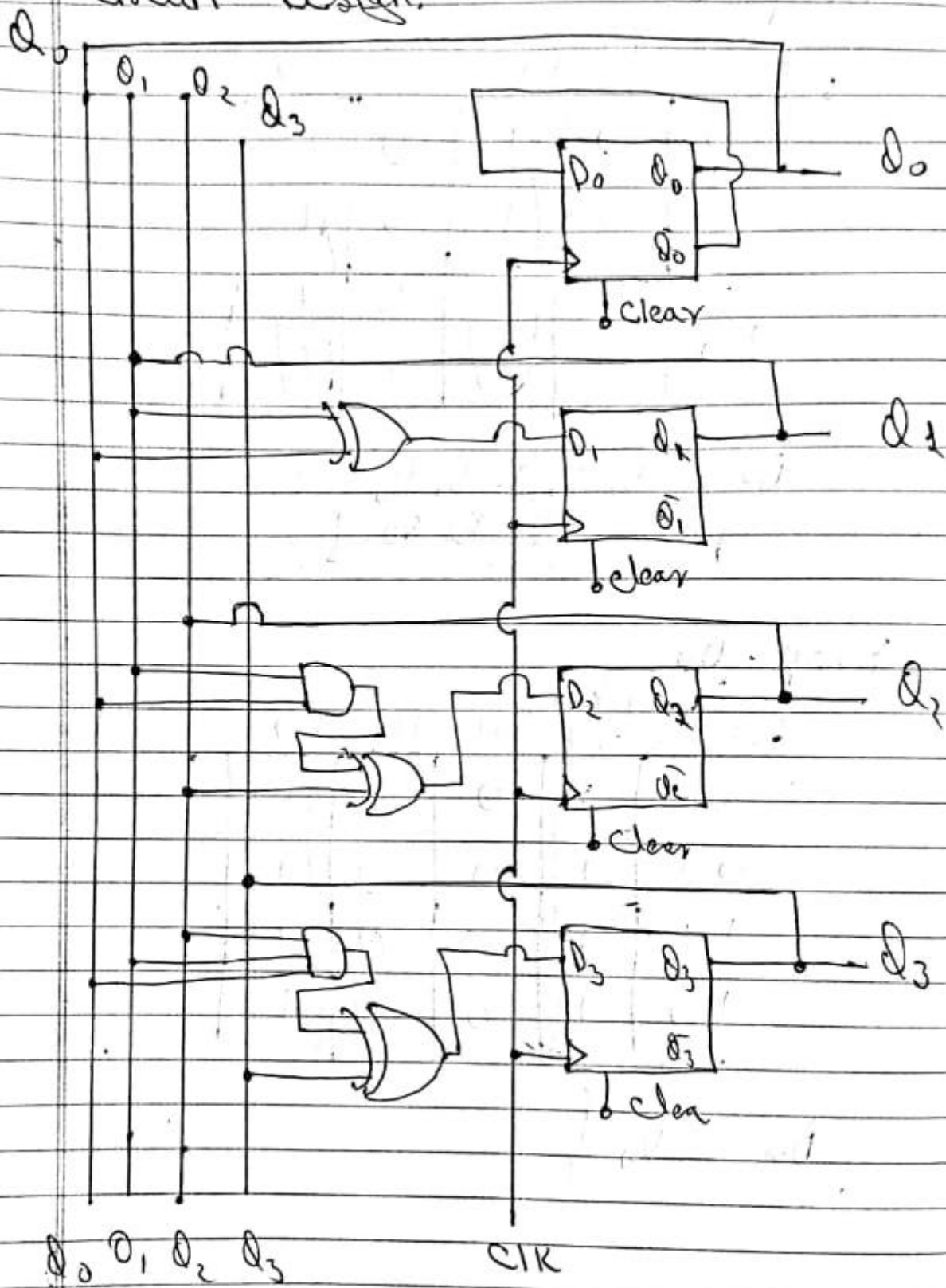

Verilog Code

```
1  `timescale 1ns / 1ps
2  module D_Flip_Flop(Q, Q_bar, D, clk, reset);
3  input clk, reset, D;
4  output reg Q;
5  output Q_bar;
6  assign Q_bar = ~Q;
7  always @(posedge clk)
8  begin
9      if(reset)
10         Q<=1'b0;
11     else
12         Q<=D;
13     end
14 endmodule
15 // 4 bit up Counter
16 module UP_Counter_4_bit(clk,reset, Q0, Q1, Q2, Q3);
17 input clk, reset;
18 output Q0, Q1, Q2, Q3;
19 wire Q0_b, Q1_b, Q2_b, Q3_b;
20
21 wire d1, d2, d3, w1, w2;
22
23 xor x1(d1, Q0, Q1);
24 and(w1, Q0, Q1);
25 xor x2(d2,Q2, w1);
26 and(w2, Q0, Q1, Q2);
27 xor x3(d3,Q3, w2);
28
29
30 D_Flip_Flop D1(Q0, Q0_bar, Q0_bar, clk, reset);
31 D_Flip_Flop D2(Q1, Q1_bar, d1, clk, reset);
```

```
12     Q<=D;
13 end
14 endmodule
15 // 4 bit up Counter
16 module UP_Counter_4_bit(clk,reset, Q0, Q1, Q2, Q3);
17 input clk, reset;
18 output Q0, Q1, Q2, Q3;
19 wire Q0_b, Q1_b, Q2_b, Q3_b;
20
21 wire d1, d2, d3, w1, w2;
22
23 xor x1(d1, Q0, Q1);
24 and(w1, Q0, Q1);
25 xor x2(d2,Q2, w1);
26 and(w2, Q0, Q1, Q2);
27 xor x3(d3,Q3, w2);
28
29
30 D_Flip_Flop D1(Q0, Q0_bar, Q0_bar, clk, reset);
31 D_Flip_Flop D2(Q1, Q1_bar, d1, clk, reset);
32 D_Flip_Flop D3(Q2, Q2_bar, d2, clk, reset);
33 D_Flip_Flop D4(Q3, Q3_bar, d3, clk, reset);
34
35 //D_Flip_Flop D1(Q0, Q0_bar, Q0_bar, clk, reset);
36 //D_Flip_Flop D2(Q1, Q1_bar, (Q0^Q1), clk, reset);
37 //D_Flip_Flop D3(Q2, Q2_bar, (Q2^(Q1&Q0)), clk, reset);
38 //D_Flip_Flop D4(Q3, Q3_bar, Q3^(Q0&Q1&Q2), clk, reset);
39
40 endmodule
41
```


Test Bench For Verilog Code





```

1  `timescale 1ns / 1ps
2  module Clock_v;
3      reg clk, reset;
4      wire Q0, Q1, Q2, Q3;
5      // Instantiate the Unit Under Test (UUT)
6      UP_Counter_4_bit uut (
7          .clk(clk),
8          .reset(reset),
9          .Q0(Q0),
10         .Q1(Q1),
11         .Q2(Q2),
12         .Q3(Q3)
13     );
14
15     initial begin
16         clk = 0;
17         forever #1 clk = ~clk;
18     end
19     initial begin
20         reset = 1;
21         #5 reset = 1'b0;
22     end
23
24 endmodule
25
26 |


```

Schematic Diagram

 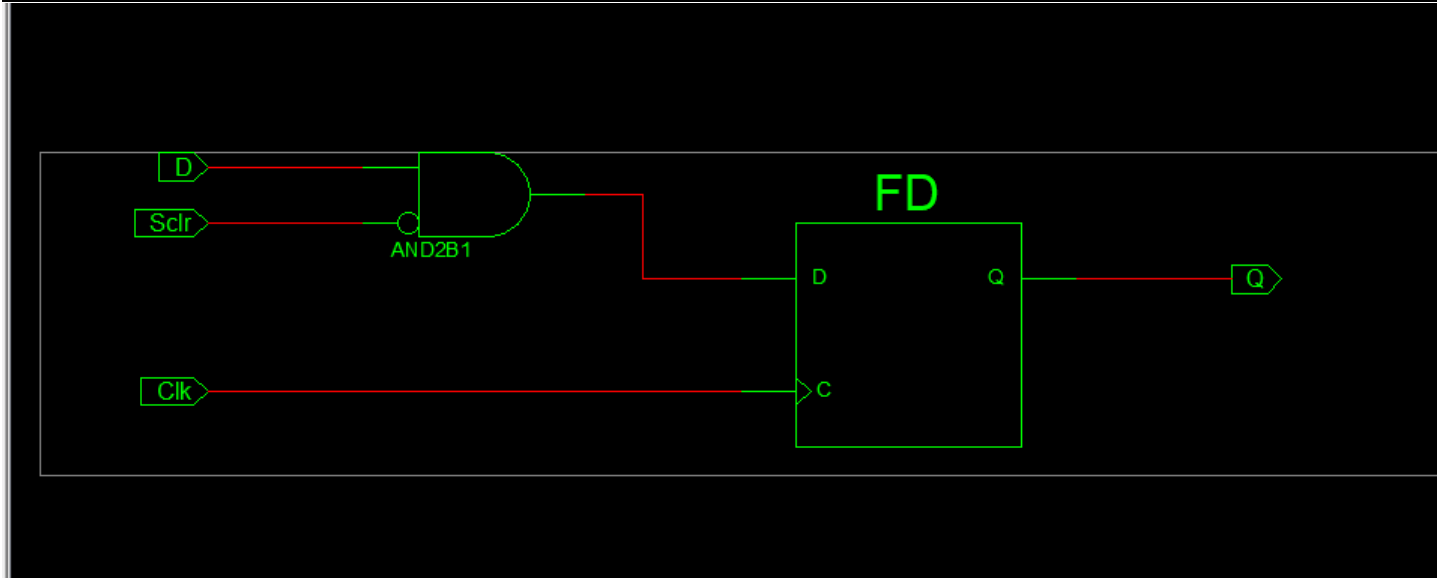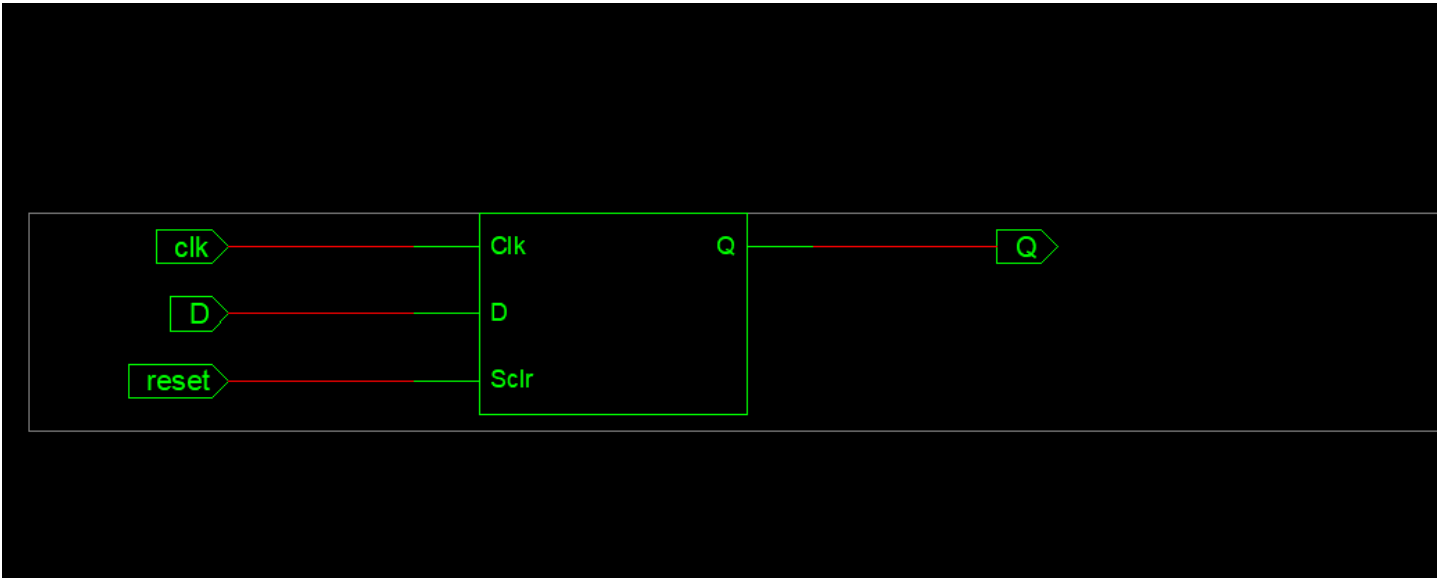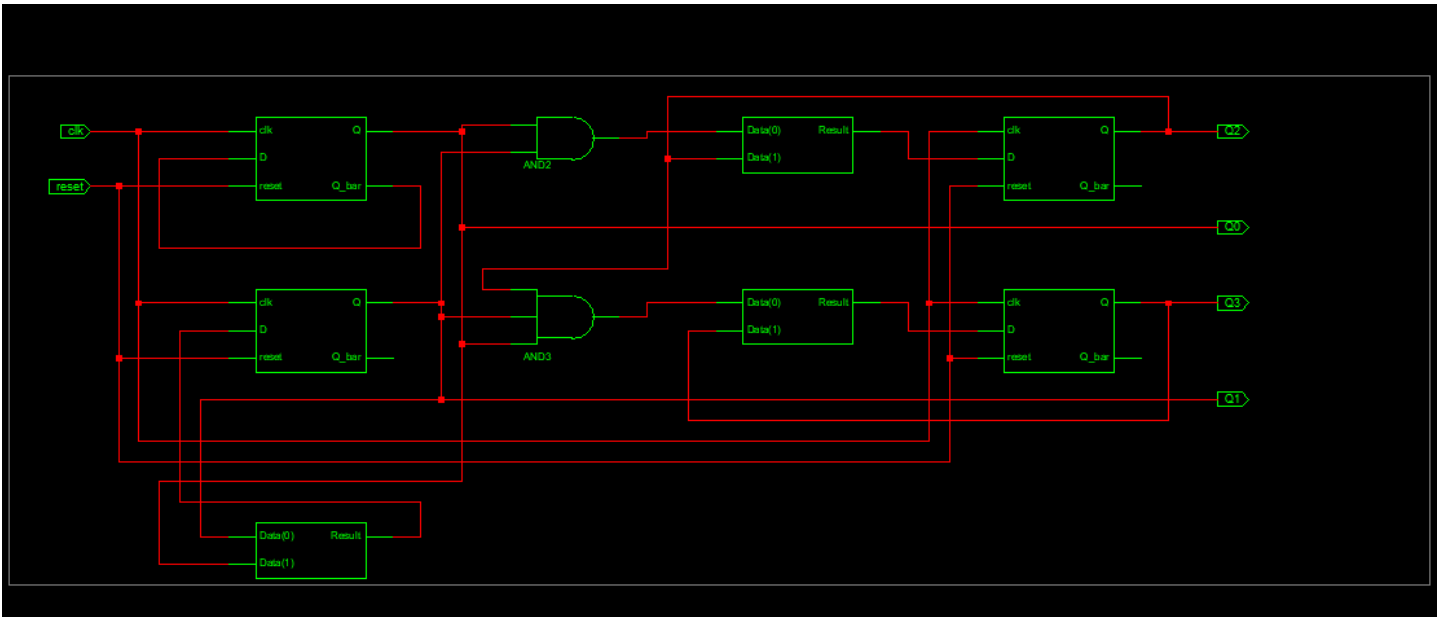



Wave Form (Output Counter)

 

END