

Assignment Submission Sheet

Term: 321221

Submission Date: 11-12-2021

Assignment Number: 06

Course Code: ECE290

Section: E1901

Group: A

Registration Number: 11904463

Student Name: Mohit Rawat

Roll No: 09

1. Concept Learned

I have learned how to make Logical gates using cmos technology and how we combine pmos and nmos to make cmos and building the logical gates. After that I have learned how to make switch level program to make cmos gates.

2. Key Observations & Insights

Key observation is the working of pull-up and pull-down networks and how we make all gates using this circuits.

3. Application Areas


Application of CMOS technology is in many place like designing gates for ICs and for other embedded systems. We makes processor and other microcontrollers using CMOS technology.

1. Draw and explain CMOS 3-input AND gate and write a Verilog code using Switch level model.
2. 2. Write a Verilog code of OR gate and NOR gate using UDP.

Name: Mohit Rawat
Section: E1901
Roll no: 09

Online Assignment- 6.

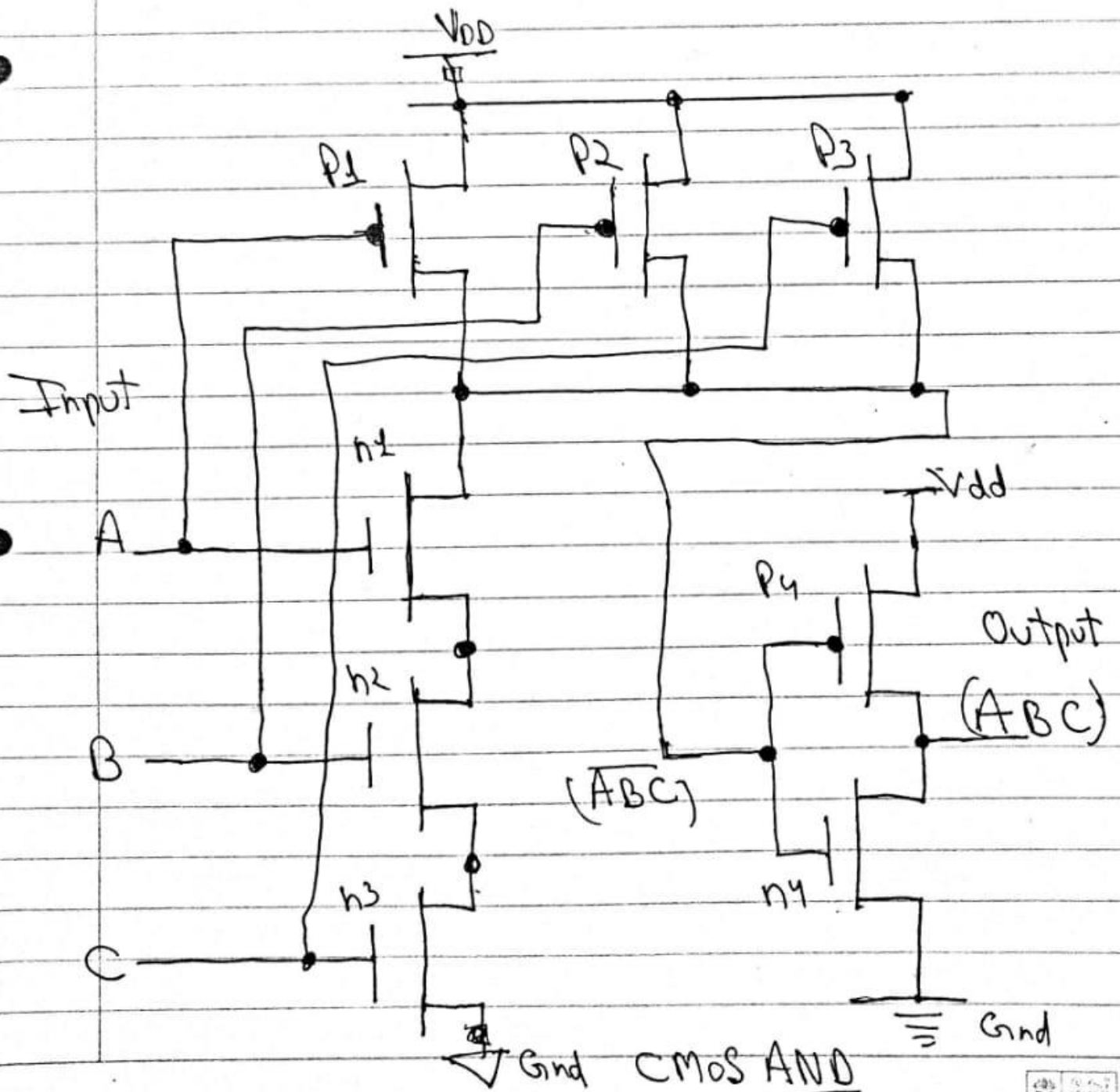Q1 Draw & explain CMOS 3-input AND gate and code.
write Switch level model.



A CMOS gate is a technology that uses one pmos which is pull-up network and connected to output 1 (V_{DD}) and other one is nmos which is pull-down network, connected to output 0 (GND). The combination of nmos & pmos makes cmos and combination of cmos we makes logical gates.

To make CMOS AND, we use 4-pmos and 4 nmos. In the diagram drawn in previous page, first 3 pmos are connected in parallel and upper end is source which is connected to supply in. 3 nmos are connected in series and last portion is connected to ground. After combining this nmos & pmos, both are connected in series. Now it become 3-Input NAND. To make it AND Gate, we use NOT Gate. 1 nmos & 1 pmos is connected in series to make Not Gate. The output of NAND Gate is connected to NOT Gate so now both combined make one AND Gate of 3-input.


Topic _____

Date _____

Function Table for CMOS 3In - AND Gate

| A | B | C | n1 | p1 | n2 | p2 | n3 | p3 | A·B·C | F |
|---|---|---|-----|-----|-----|-----|-----|-----|-------|---|
| L | L | L | off | on | off | on | off | on | H | L |
| L | L | H | off | on | off | on | on | off | H | L |
| L | H | L | off | on | on | off | off | on | H | L |
| L | H | H | off | on | on | off | on | off | H | L |
| H | L | L | on | off | off | on | off | on | H | L |
| H | L | H | on | off | off | on | on | off | H | L |
| H | H | L | on | off | on | off | off | on | H | L |
| H | H | H | on | off | on | off | on | off | L | H |

Logical Symbol.

 

Verilog Code for 3-input AND Gate.

'timescale 1ns/1ps

```
module CMOSAND(A, B, C, F);  
input A, B, C; // 3 input for AND Gate  
output F; // Output function of AND.
```

```
supply1 vdd; // Supply for pmos  
supply0 gnd; // and nmos
```

```
wire Fnot, O1, O2;
```

```
pmos P1(Fnot, vdd, A);  
pmos P2(Fnot, vdd, B);  
pmos P3(Fnot, vdd, C);
```

} Pmos in parallel NAND

```
nmos N1(O2, gnd, C);  
nmos N2(O1, O2, B);  
nmos N3(Fnot, O1, A);
```

} nmos in series

```
pmos P4(F, vdd, Fnot);  
nmos N4(F, gnd, Fnot);
```

} not gat to invert
NAND gate
get AND gate

```
endmodule
```

Q2

Verilog code of OR gate using UDP.

primitive OR gate (F, A, B);
 output F;
 input A, B;


table

| // | A | B | F; |
|----|---|---|----|
| | 0 | 0 | 0 |
| | 0 | 1 | 1 |
| | 1 | 0 | 1 |
| | 1 | 1 | 1 |

endtable
 endprimitive.

Symbol and Truth table of OR Gate.

| A | B | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

 

Verilog Cod of NOR gate using UDP

```
primitive NOR_gate (F, A, B);
  output F;
  input A, B;
```

table

| // A | B | : F; |
|------|---|------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

endtable
endprimitive

Symbol and truth table of NOR Gate

| A | B | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

