

# **Assignment Submission Sheet**

**Term: 321221**

**Submission Date: 28-09-2021**

**Lecture Date: 15-09-2021**

**Assignment Number: 02**

**Course Code: ECE290**

**Section: E1901**

**Group: A**

**Registration Number: 11904463**

**Student Name: Mohit Rawat**

**Roll No: 09**

## **1. Concept Learned**

I have learned how to make half adder and full adder using verilog and how to make 3-bit ripple carry adder that adds 3 bit number and make wave form of input and output signal.

## **2. Key Observations & Insights**

My key observation was how ripple carry adder adds two number and gives result and how our test bench make output form of output given by 3-bit ripple carry adder.

## **3. Application Areas**

The application of adder is in ALU of processor. This is unit of processor where all mathematical operation done and addition is basic process of ALU. It use addition to for subtraction, division and multiplication like operation.

## **4. A)**

**Half Adder/ Full Adder**

## **B)**

**3-bit ripple carry adder using half adder / full adder.**

## Half - Adder

1  
a) Implement Half Adder/Full adder using gate level Modelling.

Half Adder.

Truth table:

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

K-map


	$\bar{B}$	B
$\bar{A}$	0	1
A	1	0

	$\bar{B}$	B
$\bar{A}$	0	0
A	0	1

$$S = \bar{A}B + A\bar{B} \\ = A \oplus B$$

$$C = A \cdot B$$

Gate Design:

 



## Verilog Code

```
1  `timescale 1ns / 1ps
2
3  module mohit(
4      input A, B,
5      output S, C
6  );
7
8
9  xor (S, A, B);
10 and (C, A, B);
11
12 endmodule
13
14 |
```


## Test bench code

```
1  `timescale 1ns / 1ps
2
3  module rawat();
4  reg A, B;
5  wire S, C;
6
7  mohit(A, B, S, C);
8
9  initial
10     begin
11         A=0; B=0; #20;
12         A=0; B=1; #20;
13         A=1; B=0; #20;
14         A=1; B=1; #20;
15     end
16
17 endmodule
18
19
```

## Circuit design

  

## Wave form

 

## Full adder

Full Adder:-

Truth Table.

A	B	C <sub>in</sub>	S	C <sub>o</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

K-Map.

	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$	Sum
$\bar{A}$	0	1	0	1	
A	1	0	1	0	


$$S = A \oplus B \oplus C$$

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$	Carry
$\bar{A}$	0	0	1	0	
A	0	1	1	1	

$$C_o = A \cdot C_{in} + B \cdot C_{in} + A \cdot B$$

or  $C_{in} \cdot A \cdot B + C_{in} \cdot (A \oplus B)$

Gate Design

 

## Verilog Code

```
1  `timescale 1ns / 1ps
2
3  module mohit(
4      input A, B, Cin,
5      output S, Cout
6  );
7
8  wire w1, w2, w3;
9
10 and (w1, A, Cin);
11 and (w2, B, Cin);
12 and (w3, A, B);
13
14 xor (S, A, B, Cin);
15 or (Cout, w1, w2, w3);
16
17 endmodule
18
```




---

## Test bench code


```
1  `timescale 1ns / 1ps
2
3  module rawat();
4  reg A, B, Cin;
5  wire S, Cout;
6
7  mohit(A, B, Cin, S, Cout);
8
9  initial
10     begin
11         A=0; B=0; Cin=0; #20;
12         A=0; B=0; Cin=1; #20;
13         A=0; B=1; Cin=0; #20;
14         A=0; B=1; Cin=1; #20;
15         A=1; B=0; Cin=0; #20;
16         A=1; B=0; Cin=1; #20;
17         A=1; B=1; Cin=0; #20;
18         A=1; B=1; Cin=1; #20;
19     end
20
21 endmodule
22
23 |
```

---

## Circuit

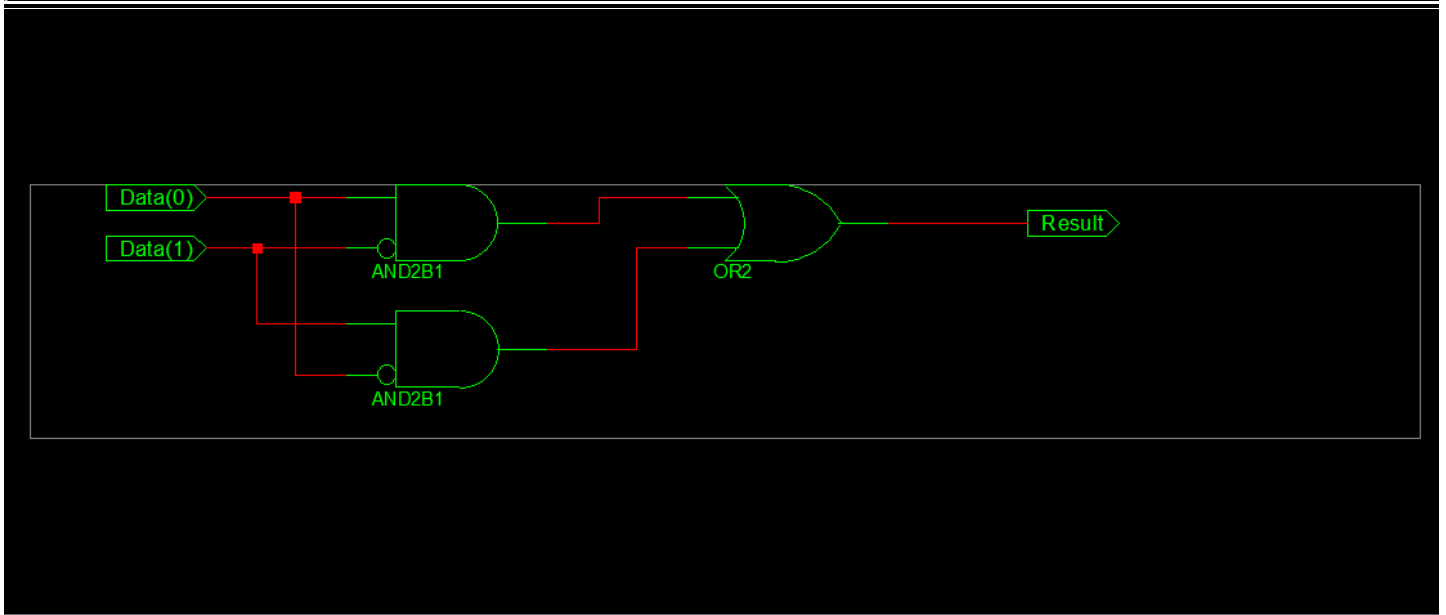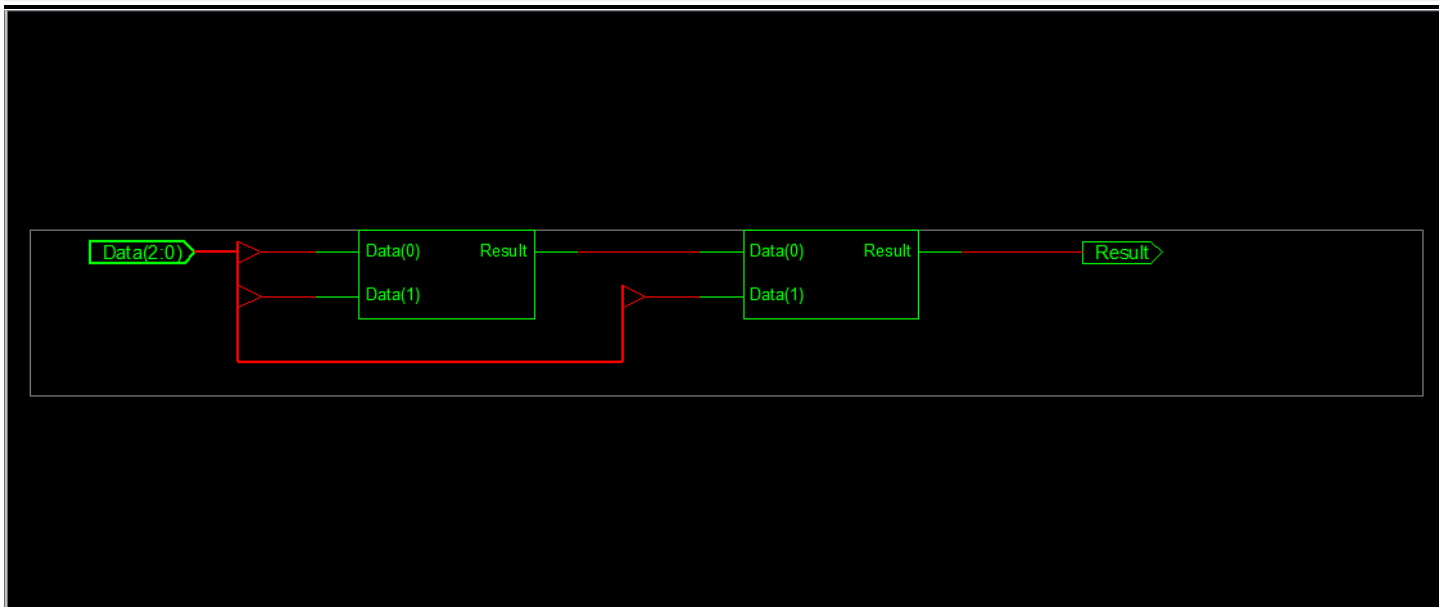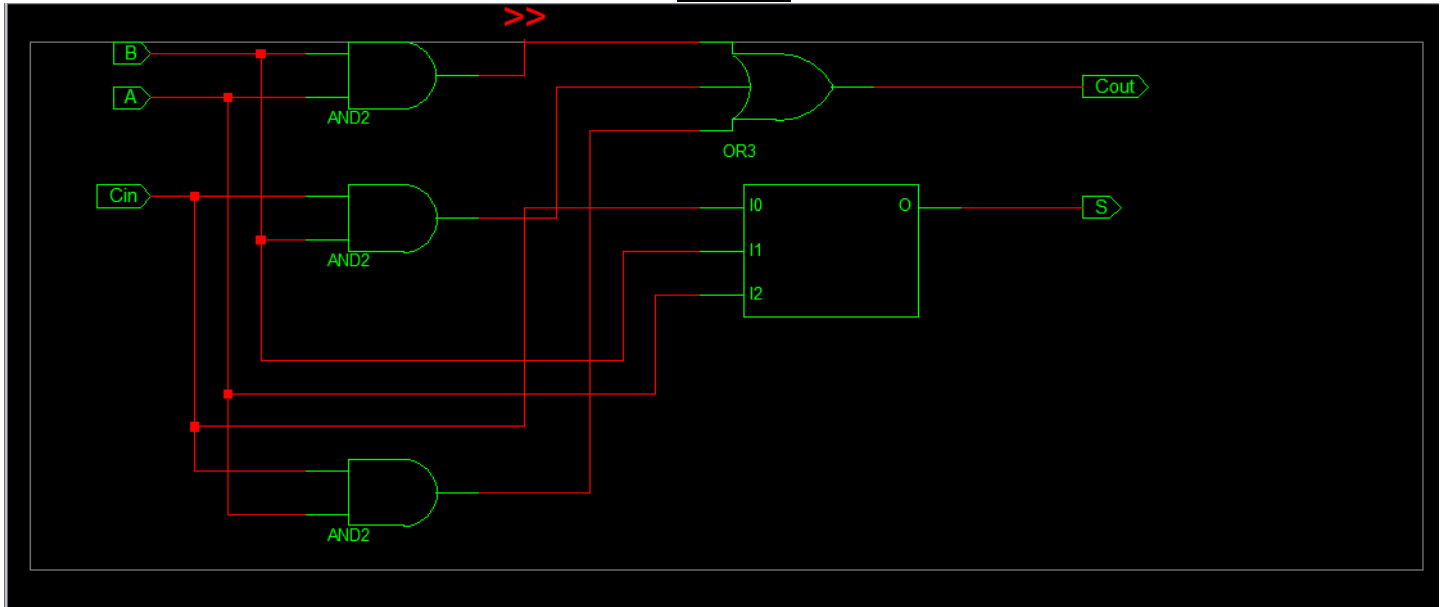

Waveform

 




### 3-bit Ripple carry Adder (using Full Adder)

b) 3-bit ripple carry adder.

Truth Table




Carry Cin	A			B			Sum			Carry Cout
	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1	0	0	0
0	0	1	1	0	1	1	1	1	0	0
0	1	0	0	1	0	0	0	0	0	1
0	1	0	1	1	0	1	0	1	0	1
0	1	1	0	1	1	0	1	0	0	1
0	1	1	1	1	1	1	1	1	0	1

Design. using Full Adder.

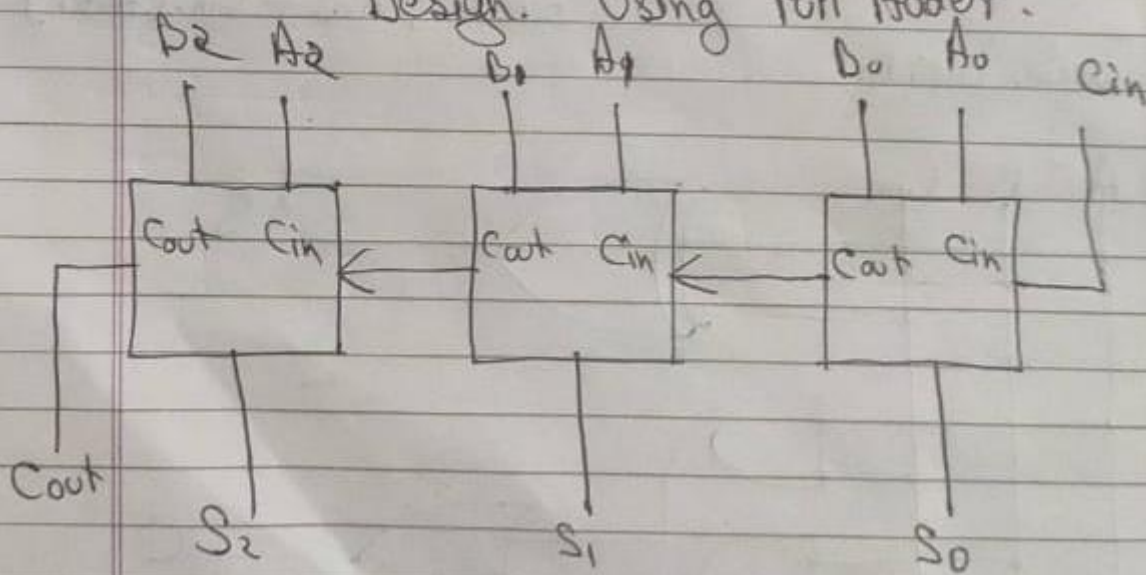

## Circuit

3-bit ripple-carry design (Full Adder)

   



## Verilog Code



```
1  `timescale 1ns / 1ps
2  module Full_Adder(A, B, Cin, S, Cout);
3  input A, B, Cin;
4  output S, Cout;
5  wire w1, w2, w3;
6  and (w1, A, Cin);
7  and (w2, B, Cin);
8  and (w3, A, B);
9  xor (S, A, B, Cin);
10 or (Cout, w1, w2, w3);
11 endmodule
12 module mohit(A, B, S, Cout);
13 input [2:0] A;
14 input [2:0] B;
15 output [2:0] S;
16 output Cout;
17 wire c0, c1;
18 Full_Adder A1(A[0], B[0], 1'b0, S[0], c0);
19 Full_Adder A2(A[1], B[1], c0, S[1], c1);
20 Full_Adder A3(A[2], B[2], c1, S[2], Cout);
21 endmodule
22
```

## Test bench Program


```
1  `timescale 1ns / 1ps
2
3  module mytb();
4  reg [2:0] A;
5  reg [2:0] B;
6  wire [2:0] S;
7  wire Cout;
8
9  mohit ad(A, B, S, Cout);
10
11 initial begin
12 A=3'b000; B=3'b000; #100;
13 A=3'b001; B=3'b001; #100;
14 A=3'b010; B=3'b010; #100;
15 A=3'b011; B=3'b011; #100;
16 A=3'b100; B=3'b100; #100;
17 A=3'b101; B=3'b101; #100;
18 A=3'b110; B=3'b110; #100;
19 A=3'b111; B=3'b111; #100;
20 end
21 endmodule
22
```

## Circuit Diagram

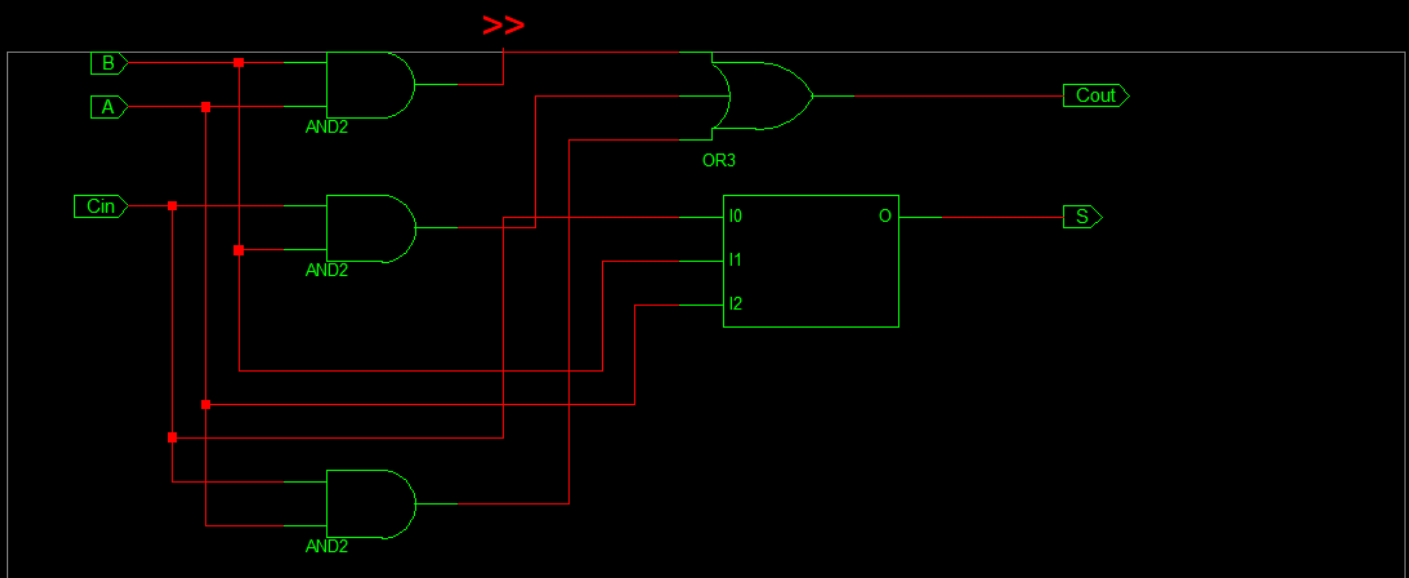 

  


## Waveform

 

**3-bit Ripple Carry Adder(Using Half Adder)**

Using half-Adder.

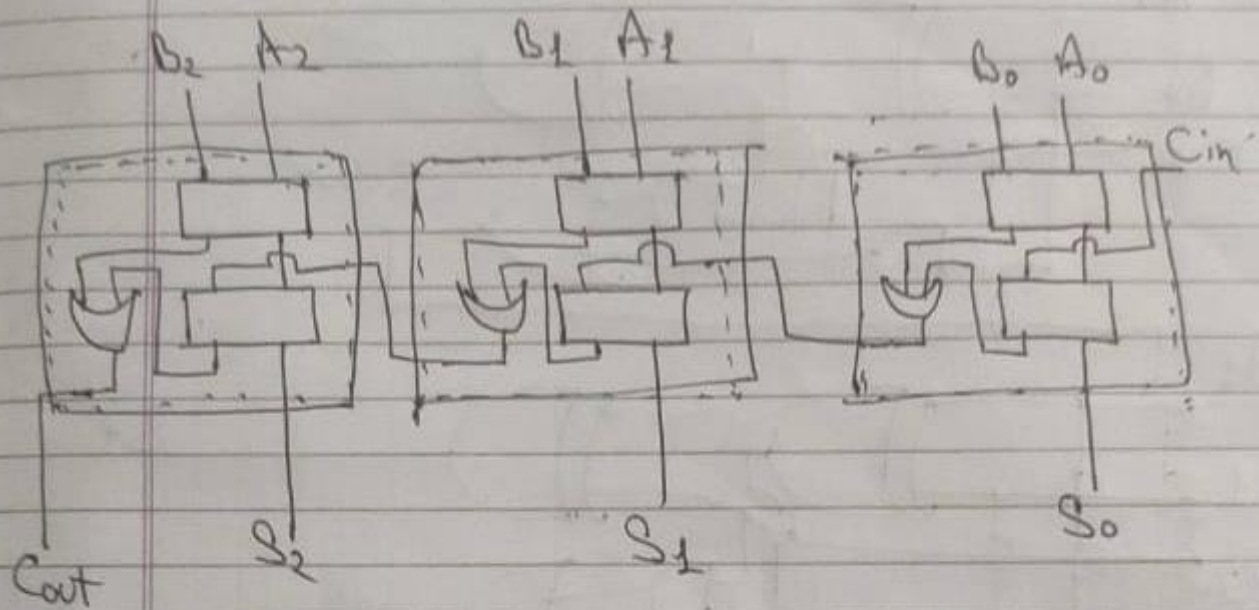


3-bit ripple Carry using Half-adder.

		$S_0$				$S_1$			
		$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$
$\overline{A}$		0	0	0	0	0	1	1	0
$A$		0	0	0	0	0	1	1	0


		$S_2$				Carry			
		$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$	$\overline{B}C_{in}$
$\overline{A}$		0	0	1	1	0	0	0	0
$A$		0	0	1	1	1	1	1	1

 $S_0 = 0$   
 $S_1 = C_{in}$   
 $S_2 = B$   
 $Carry_{out} = A$




 
### 3-bit ripple-carry design (Half Adder)



Verilog code



```

1  `timescale 1ns / 1ps
2  module Half_Adder(A, B, S, C);
3  input A;
4  input B;
5  output S;
6  output C;
7  xor (S, A, B);
8  and (C, A, B);
9  endmodule
10 module Full_Adder(A, B, Cin, S, Cout);
11 input A, B, Cin;
12 output S, Cout;
13 wire c1, c2;
14 Half_Adder h1(A, B, s1, c1);
15 Half_Adder h2(s1, Cin, S, c2);
16 or c1(Cout, c1, c2);
17 endmodule
18 module mohit(
19     input [2:0] A,
20     input [2:0] B,
21     output [2:0] S,
22     output Cout
23 );
24
25 wire c0, c1;
26 Full_Adder A1(A[0], B[0], 1'b0, S[0], c0);
27 Full_Adder A2(A[1], B[1], c0, S[1], c1);
28 Full_Adder A3(A[2], B[2], c1, S[2], Cout);
29 endmodule
30

```



## Test bench code



```

1  `timescale 1ns / 1ps
2
3  module myTB();
4  reg [2:0] A;
5  reg [2:0] B;
6  wire [2:0] S;
7  wire Cout;
8
9  mohit adH(A, B, S, Cout);
10
11 initial begin
12 A=3'b000; B=3'b000; #100;
13 A=3'b001; B=3'b001; #100;
14 A=3'b010; B=3'b010; #100;
15 A=3'b011; B=3'b011; #100;
16 A=3'b100; B=3'b100; #100;
17 A=3'b101; B=3'b101; #100;
18 A=3'b110; B=3'b110; #100;
19 A=3'b111; B=3'b111; #100;
20 end
21 endmodule
22

```

## Circuit Diagram

  

  

Waveform

Current Simulation Time: 1000 ns		475.3									
			400			600			800		1000
Cout	1										
S[2:0]	3'h0	3'h6	3'h0	3'h2	3'h4	3'h6	3'h6	3'h6	3'h6	3'h6	3'h6
A[2:0]	3'h4	3'h3	3'h4	3'h5	3'h6	3'h6	3'h6	3'h6	3'h6	3'h6	3'h6
B[2:0]	3'h4	3'h3	3'h4	3'h5	3'h6	3'h6	3'h6	3'h6	3'h6	3'h6	3'h6